
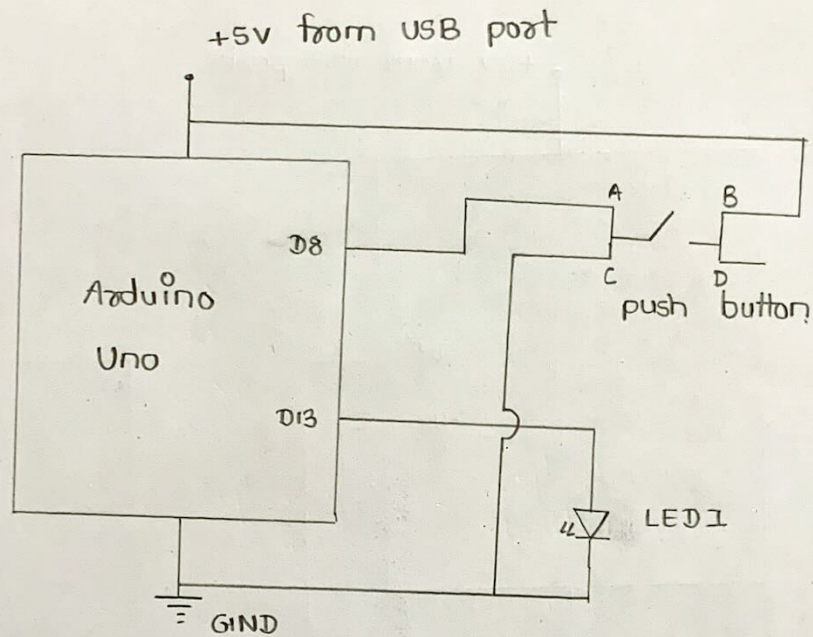


## Experiment No. 02

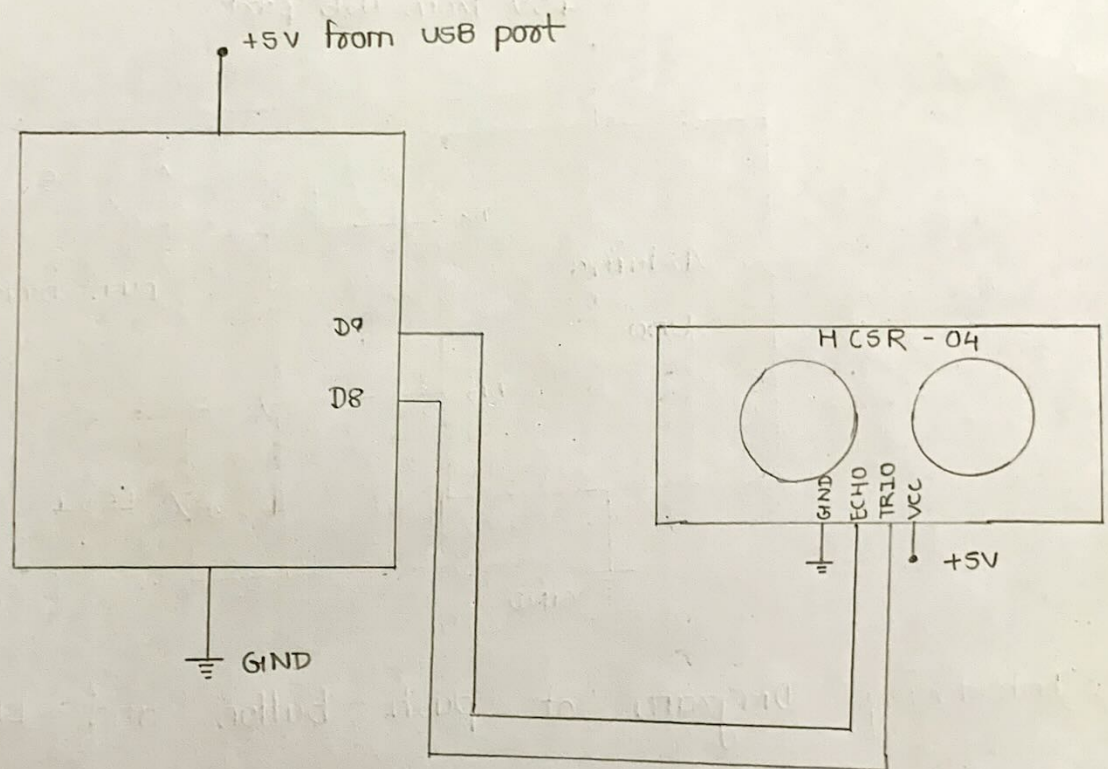


Interfacing Diagram of push button and LED with  
Arduino Uno.

## Experiment No. 02



Interfacing Diagram of Ultrasonic Distance  
sensor with Arduino Uno.


Experiment No. 03

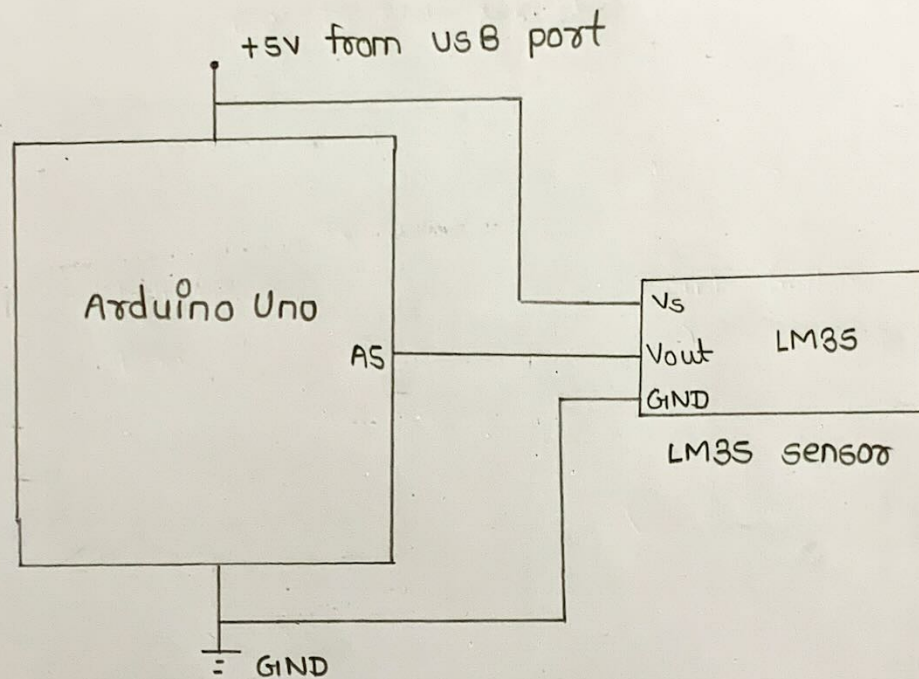

Interfacing Diagram of LM35 with Arduino Uno.




## Experiment No. 04

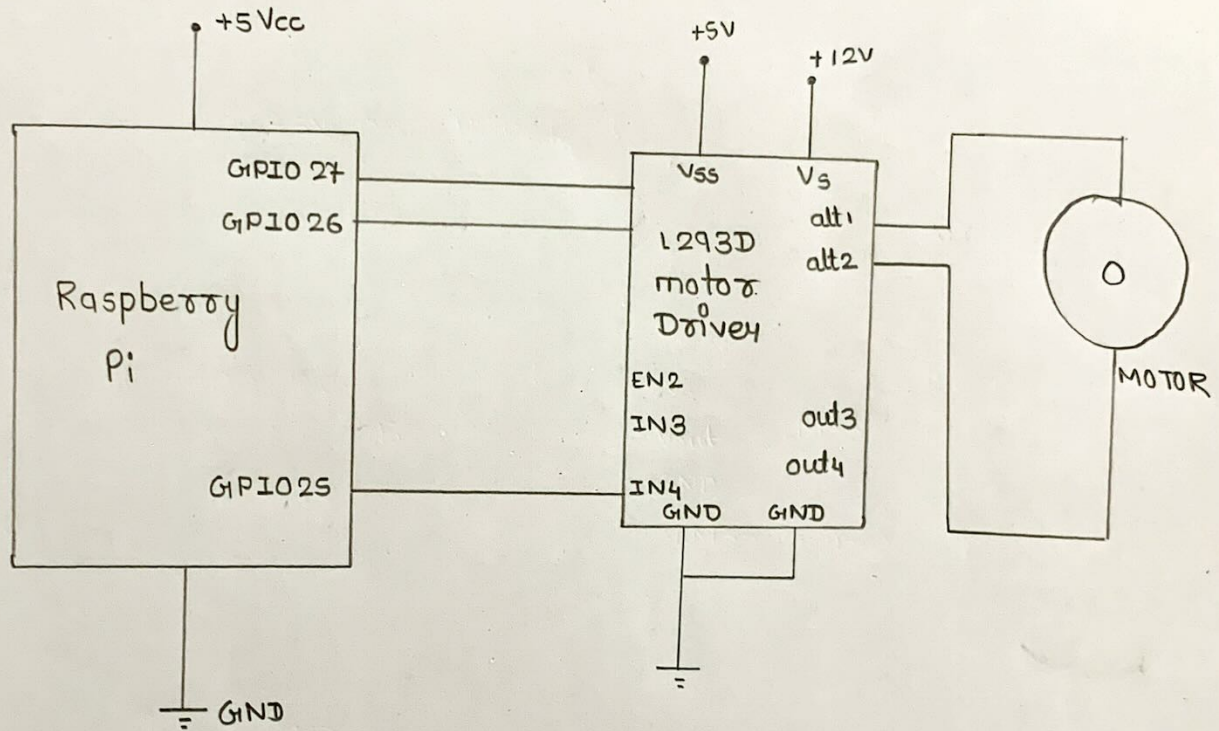

Interfacing DC motor with Raspberry Pi.


## Experiment No. 05

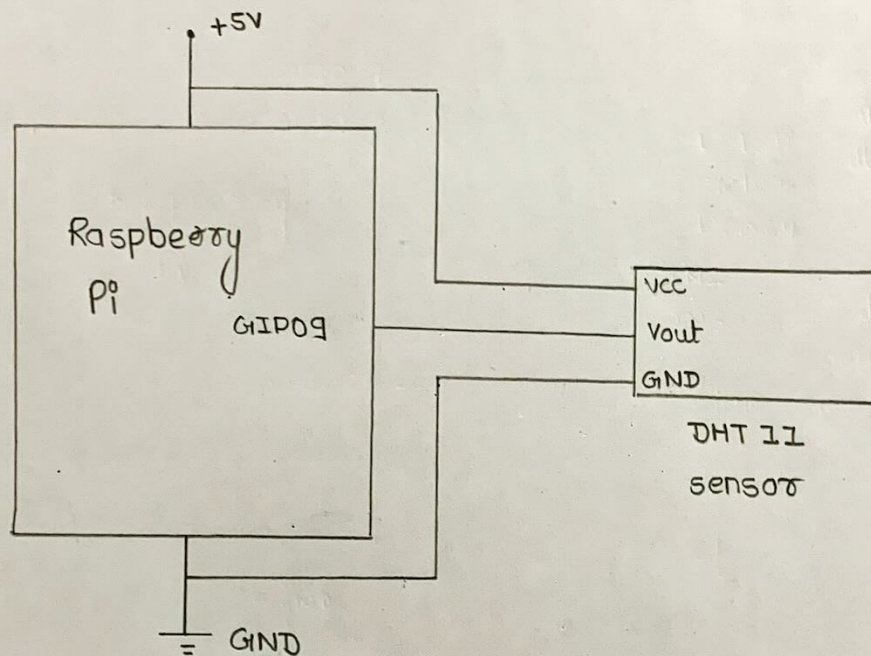

Interfacing DHT11 sensor with Raspberry Pi



## Experiment No. 07

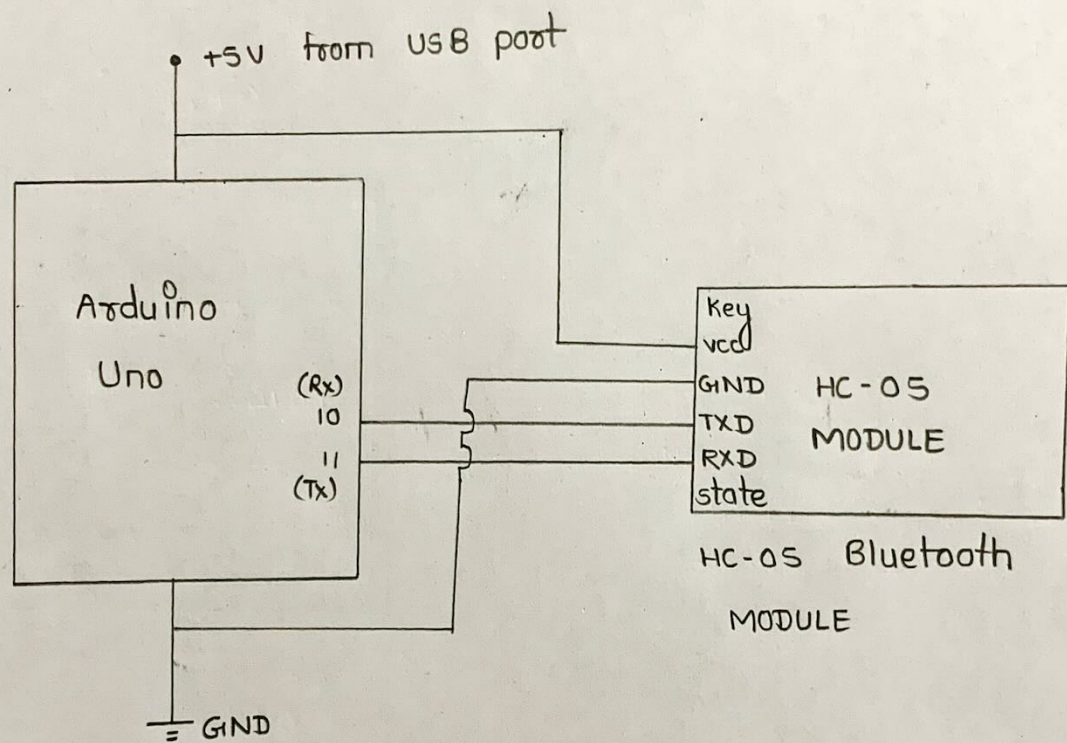

Interfacing Diagram of HC-05 Bluetooth module  
with Arduino

## Experiment No. 08

